VIETNAM NATIONAL UNIVERSITY HO CHI MINH CITY HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY FACULTY OF ELECTRICAL AND ELECTRONICS ENGINEERING



LABORATORY REPORT

Waveform generator

SUPERVISOR: Nguyễn Tuấn Hùng

SUBJECT: Digital signal processing on FPGA

GROUP: 08

List of Members

STT	MSSV	Họ Và Tên	Lớp
1	2213874	Nguyễn Thanh Tùng	L01
2	2210780	Nguyễn Đại Đồng	L01
3	2213496	Nguyễn Quốc Tín	L01

Ho Chi Minh, ../../20..

Contents

т на	araware	design and implementation	1
1.1	Modu	le Waveform Generator	1
	1.1.1	Module Sine Waveform	1
	1.1.2	Module Square Waveform	2
	1.1.3	Module Triangle Waveform	3
	1.1.4	Module Sawtooth Waveform	3
	1.1.5	Module ECG Waveform	4
	1.1.6	Module Waveform Generator	5
1.2	2 Modu	le Control value	6
		igures	
1.1	Block	diagram for Module Sin_Wave	1
1.2	2 Block	diagram for Module Square_wave	2
1.3	Block	diagram for Module Triangle_wave	3
1.4	Block	diagram for Module Sawtooth_wave	3
1.5	Block	diagram for Module ECG_wave.	4
1.6	Block	diagram for Module Waveform Generator	5
1.7	Comm	nunication operations between the user and the Control Value Module	6
1.8	Block	diagram for Module Control value	7

List of Tables

Chapter 1. Hardware design and Implementation

1.1 Module Waveform Generator

1.1.1 Module Sine Waveform

 


Figure 1.1: Block diagram for Module Sin_Wave.

DSP on FPGA Page 1 — 7

$1.1.2\ Module\ Square\ Waveform$

 


Figure 1.2: Block diagram for Module Square_wave.

DSP on FPGA Page 2-7

1 HARDWARE DESIGN AND IMPLEMENTATION

1.1.3 Module Triangle Waveform

 


Figure 1.3: Block diagram for Module Triangle_wave.

1.1.4 Module Sawtooth Waveform

 


Figure 1.4: Block diagram for Module Sawtooth_wave.

DSP on FPGA Page 3 — 7

1 HARDWARE DESIGN AND IMPLEMENTATION

1.1.5 Module ECG Waveform

 


Figure 1.5: Block diagram for Module ECG_wave.

DSP on FPGA Page 4-7

1.1.6 Module Waveform Generator

 


Figure 1.6: Block diagram for Module Waveform Generator.

DSP on FPGA Page 5-7

1.2 Module Control value

 


Figure 1.7: Communication operations between the user and the Control Value Module.

DSP on FPGA Page 6 — 7

 


Figure 1.8: Block diagram for Module Control value.

DSP on FPGA Page 7-7